

(Set-R₁)

B.Tech-6th
Power Electronics

Full Marks : 70

Time : 3 hours

Answer Q. No. 1 is compulsory and five questions from the rest

The figures in the right-hand margin indicate marks

1. Answer the following questions : 2 × 10

- (a) What are the protections needed for an SCR ?
- (b) What is the purpose of using freewheeling diode in a ac-dc controlled converter ?
- (c) How many SCRs are conducting during overlap period in case of a 1-phase full wave converter ?
- (d) What will be firing angle of an 230V 1-phase full-controlled converter feeding a resistive load with 100V ?

(e) What will be output RMS voltage when an triac is fired with angle " α " ?

(f) What is the difference between IGBT and IGCT ?

(g) What is the necessity of source inductor in case of a CSI ? What are the drawbacks of CSI ?

(h) Draw an R-C triggering scheme. What will be maximum firing angle of this scheme ?

(i) What is the advantage of a chopper operating under fixed frequency control ?

(j) What is the objective of using UJT in triggering scheme ?

2. (a) Draw an cosine-law triggering scheme and explain its working principle. 5

(b) Discuss briefly about IGBT with $V \sim I$ characteristic. 5

3. (a) What do you mean by forced commutation ? Discuss briefly about current commutation with its relevant waveforms. 5

(Turn Over)

B.Tech-6th/Power Electronics (Set-R₁)

(Continued)

- (b) Derive rms voltage of an triac feeding a resistive load. Which type of firing scheme will be required for triac control ? 5
4. A single-phase 250V, 50 Hz half-controlled bridge converter provides a ripple-free load current of 10A at firing angle of 30 degree.
- (a) Draw the circuit diagram and its voltage and current waveforms of both load and source side. 4
- (b) Find the average output voltage, RMS input current, displacement and distortion factor. 6
5. (a) Derive the expression of average load current in terms of ' α ' and ' μ ' for a single-phase fully-controlled converter having source inductance " L_s " feeding ripple free load current. 5
- (b) Explain the operation of a 1-phase series inverter and its limitations and modifications. 5
6. (a) Draw an 1-phase cyclo-converter and explain its operation. What modification is needed to improve the fundamental output ? 5

(Turn Over)

- (b) Draw circuit diagram of a 1-phase CSI. Explain its operation with load voltage and current waveforms. 5
7. (a) Draw an 3-phase bridge inverter feeding balanced load and its phase and line voltage when it is operating under 180 degree mode. 5
- (b) Explain four-quadrant operation of chopper. 5
8. Write short notes on any two of the following : 5 + 5
- (i) UJT triggering scheme
- (ii) Step-up chopper
- (iii) Series and parallel connection of SCRs.

<http://www.odishastudy.com>

Whatsapp @ 9300930012

Send your old paper & get 10/-

अपने पुराने पेपर्स भेजे और 10 रुपये पायें,

Paytm or Google Pay से